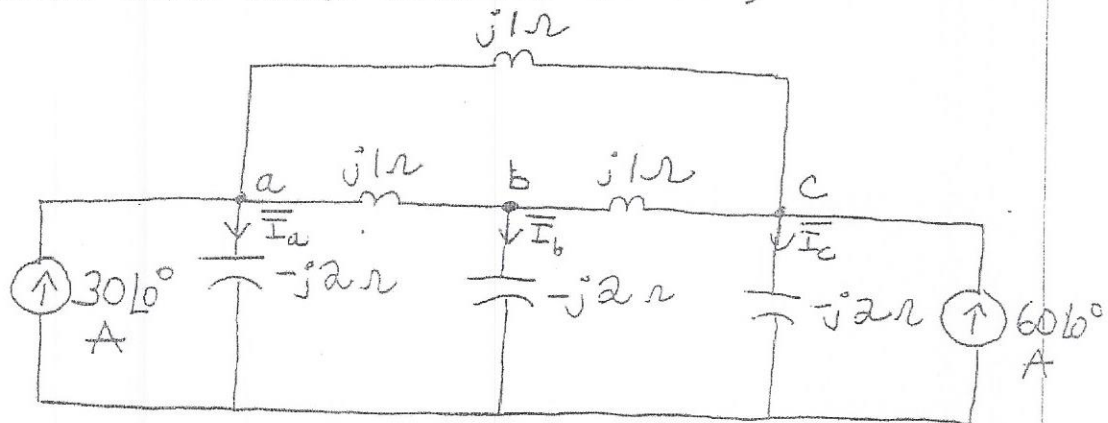


H.W. #9 Due: Wed., April 8

#1) Given theckt. shown below,



a.) Use the fact that

$Y_{ii} = \text{sum of admittances directly connected to node } i$

$Y_{ij} = -(\text{sum of admittances connected between nodes } i \text{ and } j)$


to write down the nodal equations in matrix form.

b.) Find \bar{V}_a , \bar{V}_b , \bar{V}_c using symmetrical components.

c.) Now find \bar{I}_a , \bar{I}_b , and \bar{I}_c .

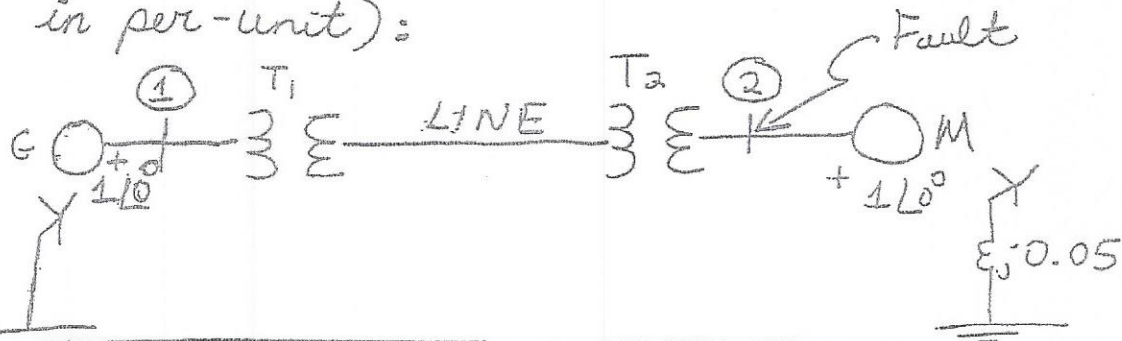
#2)

For the system shown below (all values in per-unit):



	\bar{Z}_0	\bar{Z}_1	\bar{Z}_2
Generator	$j0.05$	$j0.15$	$j0.17$
Motor	$j0.10$	$j0.20$	$j0.21$
Transf. 1	$j0.10$	$j0.10$	$j0.10$
Transf. 2	$j0.10$	$j0.10$	$j0.10$
Line	$j0.105$	$j0.105$	$j0.105$

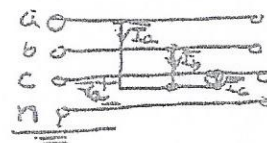
- Draw the positive-sequence network and determine the Thevenin equivalent from bus (2) to ground.
- Calculate the fault voltage and the fault current for a symmetrical fault at bus (2), with $\bar{Z}_F = 0$ (bolted short).
- Calculate \bar{I}_a for this 3 ϕ fault. Also calculate \bar{I}_b and \bar{I}_c .



#3)

The diagram below represents the Thevenin equivalent of a single-phase distribution system. A fault occurs between point X and ground. R_F represents the fault resistance. The current I_F is 3,600 A when R_F is 0 Ω . If R_F is changed to 1.0 Ω , the current I_F (amperes) is most nearly:

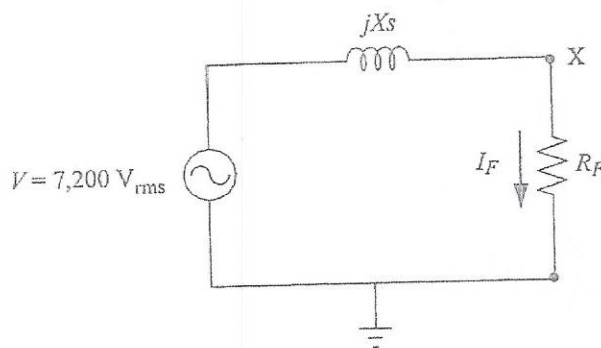- (A) 2,000
- (B) 2,400
- (C) 3,200
- (D) 4,600




#4.)

Consider the 60-kV transmission system below. Transmission line impedances are:

$$Z_1 = 16.75 \angle 71^\circ \Omega$$


$$Z_2 = 13.4 \angle 71^\circ \Omega$$

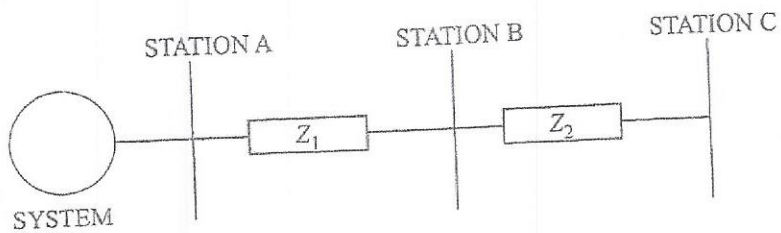

With a system impedance of $13.25 \angle 81^\circ \Omega$, the 3-phase fault current (amperes) at Station C is most nearly:

- (A) 2,590
- (B) 1,495
- (C) 1,285
- (D) 800
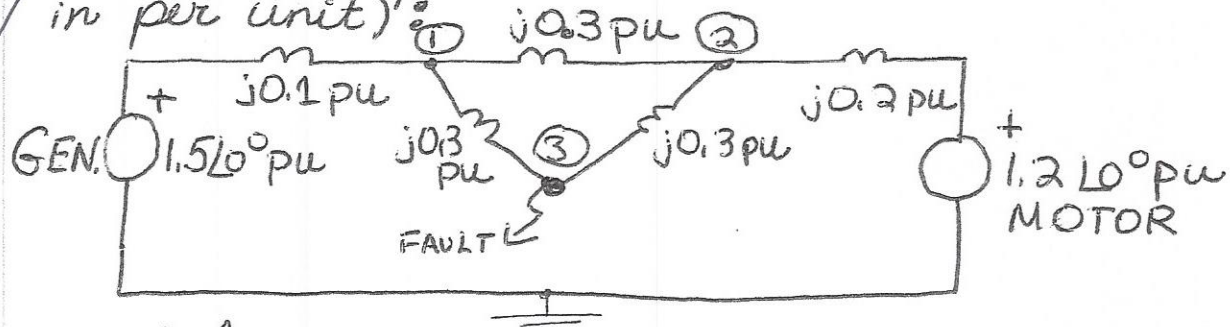
#5) For the system shown below (all values in per unit):



- Redraw the ckt. with the Δ changed to Y. See Hint
- Using the ckt. obtained in a, determine the Thevenin equivalent from bus ③ to ground.
- Calculate the fault voltage and the fault current for a symmetrical fault at bus ③ with $\bar{Z}_F = j0.01 \text{ pu}$.
- Calculate the fault current through each one of the two machines. Let \bar{I}_{g1} and \bar{I}_{m1} be these currents. If $\bar{I}_{g1} = \bar{I}_{ag}$, what is \bar{I}_{bg} and \bar{I}_{cg} ? If $\bar{I}_{m1} = \bar{I}_{am}$, what is \bar{I}_{bm} and \bar{I}_{cm} ?

